

Carry Look Ahead Adders

- In order to reduce the propagation delay and overflow in ripple adders, the concept of **Carry Look Ahead Adder** (a binary parallel adder) is generated.

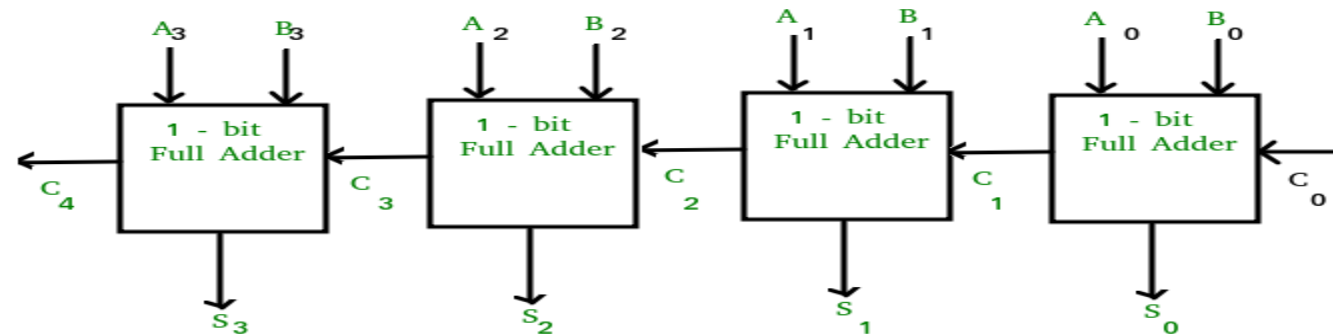


Figure: A 4 bit ripple carry adders

- In ripple carry adders, each adder depends (waits for the carry to arrive in) on its previous adder to produce output.
- Thus each adder experiences a certain amount of increasing delay. For long numbers, which become unacceptably high.

Carry Look Ahead Adders_(contd.)

- Here, the carry input signals are generated directly from the inputs instead of the ripple arrangement. So, each single bit adder can function independently.
 - To generate a carry input for each adder, the following expressions are carried out:
$$C_0 = A_0 B_0$$
$$C_1 = A_1 B_1 + A_1 A_0 B_0 + B_1 A_0 B_0$$
$$C_2 = A_2 B_2 + A_2 A_1 B_1 + A_2 A_1 A_0 B_0 + A_2 B_1 A_0 B_0 + B_2 A_1 B_1 + B_2 A_1 A_0 B_0 + B_2 B_1 A_0 B_0$$
- Thus, each carry can be expressed as a SOP form from the inputs directly with no previous carry.
- Only two levels of delay occur here regardless of the length of the adder.
- The advantage is that the length of time it requires to produce the correct SUM does not depend on the number of data bits used in the operation.
- The speed of this parallel adder is greatly improved with this carry look ahead logic.
- Typically, carry look ahead is done for 4 to 8 bits at a time, because for long numbers this approach becomes excessively complicated.

Carry Save Adder

- It is a parallel full adder that adds three (or more) numbers without any horizontal connection.
- If there are three numbers A, B, and C, then it produces two outputs sum S and carry C, and the summation is carried out by the following expression:
 - $C+S=A+B+C$.
- S and C are calculated as follows:
 - $S_i = A_i \oplus B_i \oplus C_i$ (exclusive OR operation)
 - $C_{i+1} = A_i B_i + A_i C_i + B_i C_i$ (AND and OR operations)
- For example, if A=101 ($A_2=1, A_1=0, A_0=1$), B=110 ($B_2=1, B_1=1, B_0=0$) and C=111 ($C_2=1, C_1=1, C_0=1$), Then the S and C are calculated as follows:

Carry Save Adder_(contd.)

$$A = 1\ 0\ 1$$

$$B = 1\ 1\ 0$$

$$C = 1\ 1\ 1$$

$$S = 1\ 0\ 0$$

$$C = 1\ 1\ 1$$

So the final output is =10 0 1 0

 


Figure: Carry Save Adder

Carry Save Adder_(contd.)

- The CSA is typically used in a binary multiplier because the addition of more than two numbers are involved after multiplication.
- The advantage is that it reduces the addition of three numbers to the addition of two numbers.
- It reduces propagation delay as the C and S are calculated in parallel.
- The propagation delay does not depend on the number of bits.